

ECE60420 Final Project

14-16 GHz Sliding-IF Receiver


Ryan Wans
Purdue University
Fall 2025

Sliding-IF Receivers

- Dual conversion receiver for I/Q output
- LO controls both mixers via divider
- Growing popularity for modern modulation schemes
- Usually ~20-60nm CMOS or SiGe
- Implementations up to >300 GHz

Prior Approaches:




 
- Cascode LNA, active double-balanced mixers, DFD divider(s), LO off-chip (!)



Sliding-IF Receivers

Standard Figures of Merit

 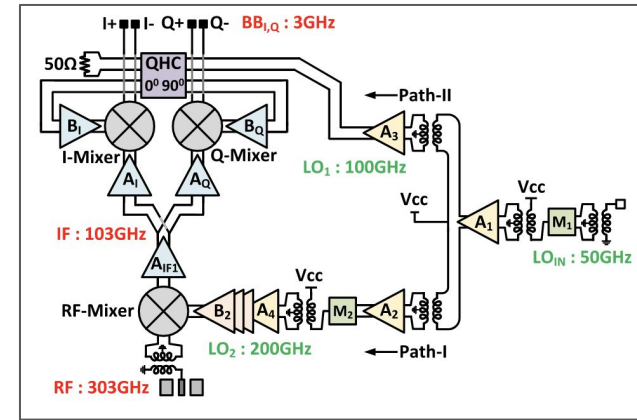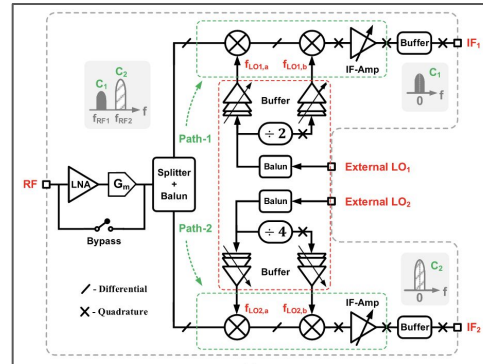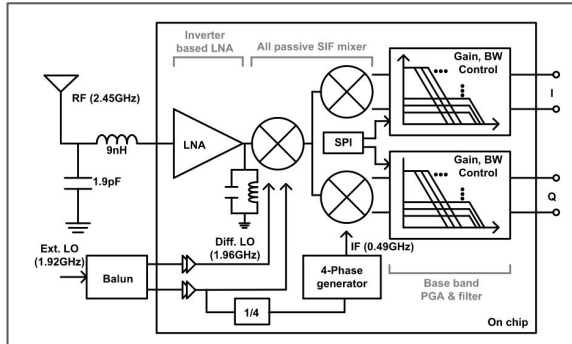- Gain (typ. > 30 dB)
- NF (typ. < 10dB)
- P1dB (typ. < 25 dBm)
- Power (typ. < 100 mW)
- Area (typ. < 1 mm²)
- LO Phase Noise (typ. < 100 dBc/Hz)



Circuit Analysis & Predictions


Low Noise Amplifier

Cascode w/ ind. degen.

NF < 1dB and Gain > 20dB

Will have to add shunt C_g

^ GPDK 45nm not super realistic

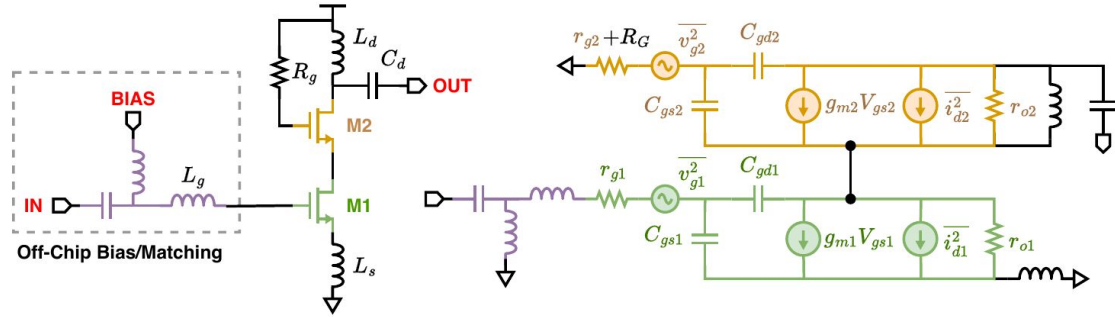


LC-VCO

Want big L for higher Q of tank, want higher C for tuning

NMOS/PMOS XCP for output Z, low I_d , negative g_m

 Output buffer to prevent loading, allow biasing/gain



Circuit Analysis & Predictions


Mixer

Double balanced, passive

High linearity, low noise, low power consumption, low complexity

Low gain: conversion loss ≥ 3.92 dB

 Output sees 2 mixers $\Rightarrow \geq 7.84$ dB of loss :(




Frequency Divider

Injection-Locked Freq. Div (ILFD)




Combined LC-VCO with passive mixer!

Fold two: allows for 4 -phase quadrature output


 
Sizing determines gain, locking range, power cons.





Circuit Design & Layout

  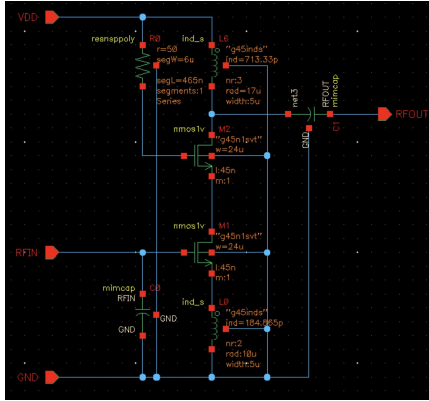

Low Noise Amplifier

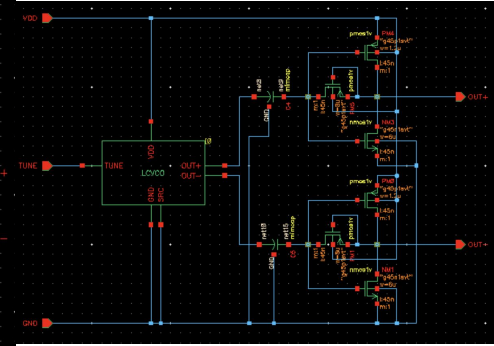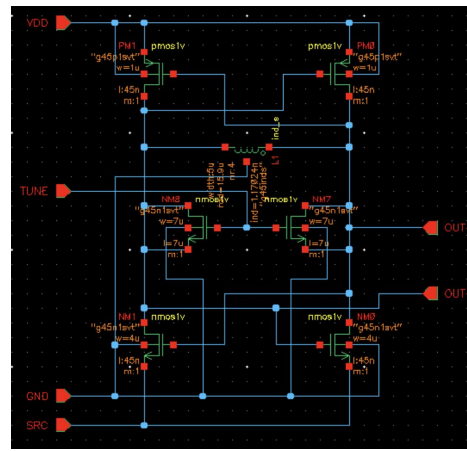






VCO

  

Circuit Design & Layout

I/Q Div-by-4 ILFD

Mixer

  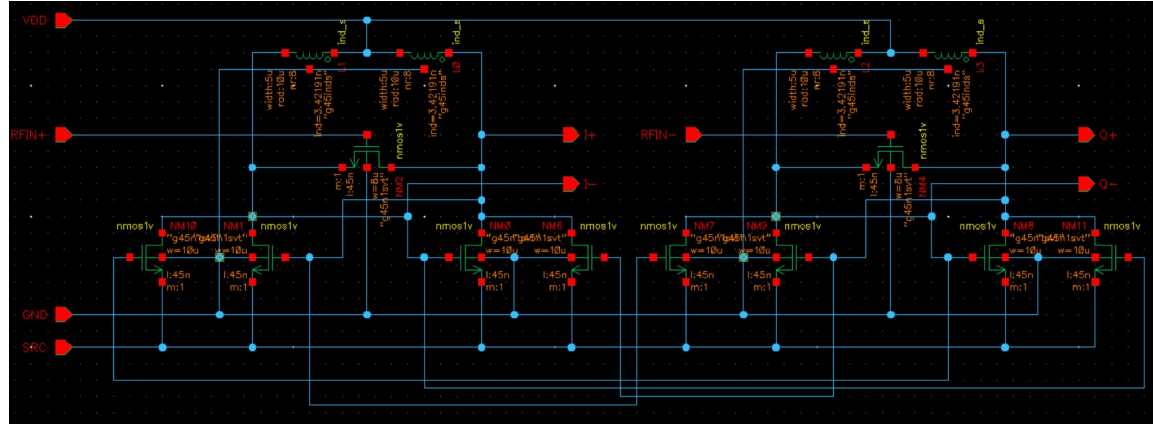 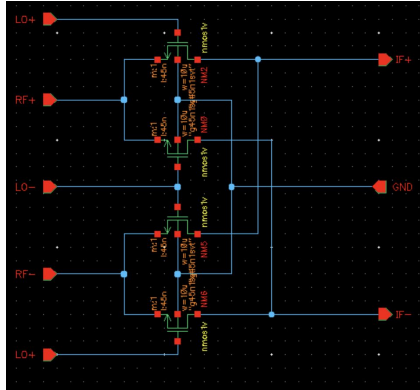

Layout DRC/LVS Results

Minor DRC errors due to poor inductor pcells

Clean :)

The screenshot displays the Cadence Virtuoso environment with the following components:

- Main Window:** Shows a circuit layout with various components and interconnects. The status bar indicates coordinates: X: 434.2900, Y: 167.6350, DX: 416.3600, DY: 124.3700, Dist: 434.5383, Cmd:.
- Left Sidebar:** Contains a 'Layers' panel with a list of layers and their purposes. The 'Active' layer is 'Nwell drawing'. The 'Layer Set' is 'All Layers'. The 'Search' filter is 'Filter'. The 'Active' layer is 'Nwell drawing'.
- Bottom-Left Window (PVS 23.11-64b DRC Results Viewer):** Shows the DRC results for the project 'ECE60420_PROJECT-SLIDING_IF_RECEIVER-layout'. The results table shows 1000 results in 1 of 562 checks. The total number of non-empty checks is 1.
- Bottom-Right Window (PVS 23.11-64b LVS Run Status):** Shows the LVS status with a green checkmark and 'Clean' results. The status is 'Clean' and the comparison results are 'Match'.
- Right Sidebar:** Contains an 'Electromagnetic Solver' panel with a table of models. The table has columns: Name, Simulator, Corner, Status. The model 'model1' is listed with simulator 'EMX', corner 'gsdk045.typ', and status 'exported'.

Simulation Results (Pre-Layout)

System

- Gain: **-9.2 dB** (no IF amplifiers, passive mixers)
- NF: **9.7/14.2 dB**
- P1dB: **-40 dB**
- Power: **188 mW**
- Input Z: **$\sim 50 + j0$ Ohms**

VCO

- LO Phase Noise: **-127 dBc/Hz**
- LO Freq. (tune = 0): **12.8 GHz**
- LO Freq. (tune = 1): **10.5 GHz**

LNA

- Center: **15 GHz**
- Gain: **21.4 dB**
- NF: **980 mdB**
- S11: **-10 dB**
- P1dB: **-22 dB**

Simulation Results (Post-Layout)

System




- Gain: **-11.5 dB** (worse)
- NF: **12/16.7 dB** (worse)
- P1dB: **-41.4 dB** (worse)
- Power: **45.8 mW** (better)
- Input Z: **18 + j34 Ohms** (worse)

VCO

- LO Phase Noise: **-101 dBc/Hz** (worse)
- LO Freq. (tune = 0): **11.5 GHz** (worse)
- LO Freq. (tune = 1): **0 GHz** :((worse)

LNA

   - Center: **14.2 GHz** (worse)
- Gain: **19.2 dB** (worse)
- NF: **1.28 dB** (worse)
- S11: **-7.9 dB** (worse)
- P1dB: **-19.2 dB** (better)



Simulation Results (EMX)

System

- Gain: **-39.4 dB**
- NF: **22.2/23.9 dB**
- P1dB: **pss divergence**
- Power: **11.4 mW**
- Input Z: **26.8 + j31 Ohms**

VCO

- LO Phase Noise: **no start**
- LO Freq. (tune = 0): **no start**
- LO Freq. (tune = 1): **no start**

LNA

- Center: **14.6 GHz**
- Gain: **6.7 dB**
- NF: **1.63 dB**
- S11: **-9.97 dB (@ 14.15 GHz)**
- P1dB: **-14.9 dB**

Conclusion

- Successfully performed sliding-IF down conversion
- Room for improvement with gain, P1dB, and power consumption
- Recommendation: active mixers or IF amplifier, optimize ILFDs

TABLE I
COMPARISON TO STATE-OF-THE-ART SLIDING-IF RECEIVERS

Ref.	Tech.	Freq. (GHz)	Gain (dB)	NF (dB)	P1dB (dBm)	Power (mW)	Area (mm ²)	LO Phase Noise (dBc/Hz) @ 10 MHz Offset
[2]	65nm	5.1-5.9	39	1.9/2.4	-28.5	72	0.56	
[3]	22nm FDSOI	28	37.5	3.5	-31	19.5		
[4]	65nm	61.5-66.5	28	9	-26	80	0.5	-115 @ 64 GHz
[6]	130nm SiGe	187-313	15.2	29.5	-17	406	2	
[7]	22nm SOI	137-156	30	9/10.5	-29	197.5	3.10	
This Work	45nm	14-16	-9.2*	9.7/14.2	-40	188[†]	0.21	-127 @ 16 GHz

*Passive mixers and no IF amplifier, [†]Includes frequency dividers